

Find the problem with Ruth's circuit



Oh no! Ruth's circuit for the Robot Burger isn't working. Can you help her figure out what's gone wrong?
Draw and **explain** how you would fix the circuit to get Robot Burger moving again.




Motor



Open Switch



Closed Switch

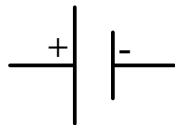

Battery



Wire

Circle the fault on the circuit	Describe what is wrong with Ruth's circuit	Draw and label a correct circuit to help Ruth fix the Burger Robot

